

# MEDIS – Module 2

Microcontroller based systems for controlling industrial processes

Lab 3.3: Amplifier Circuits

M. Seyfarth, Version 0.1

## 1.1 Objectives of the lab

1.2 Work orders

1.3 Conclusion

# Aims of the lab

- Know electric wiring for amplifier circuits
- Draw basic amplifier circuits
- Connect Sensors and Actuators to a microcontroller
- Build up simple electric circuits

1.1 Objectives of the lab

**1.2 Work orders**

1.3 Conclusion



# Work orders

1. You want to control a single traffic light (cars and pedestrians). There is one push button on each side of the road. Each color of the traffic light is a combination of 50 high power LEDs. Draw the electrical circuit to connect all sensors and actuators to a microcontroller.
2. You want to measure the temperature of an oven. You choose the sensor KTY 84-130. The range for measurement should be  $50 \dots 300^{\circ}\text{C}$ . Wire this sensor with an appropriate resistor to an analog input pin of the microcontroller.
3. You want to connect a DC-motor of 250 W (24 V supply voltage) to a microcontroller and control it with two directions of variable revolution. Draw the electric circuit and calculate the necessary elements.

1.1 Objectives of the lab

1.2 Work orders

**1.3 Conclusion**

# Conclusion

1. Know basic circuits for connection of LEDs, sensors and motors to a microcontroller.
2. Know the symbols of electric elements in circuits.